

Kevin Honeker

Embedded Systems

Lab Report 1


2/28

Purpose: The purpose of this lab was to create a sophisticated counter operated by buttons whose signals were passed through debouncers.

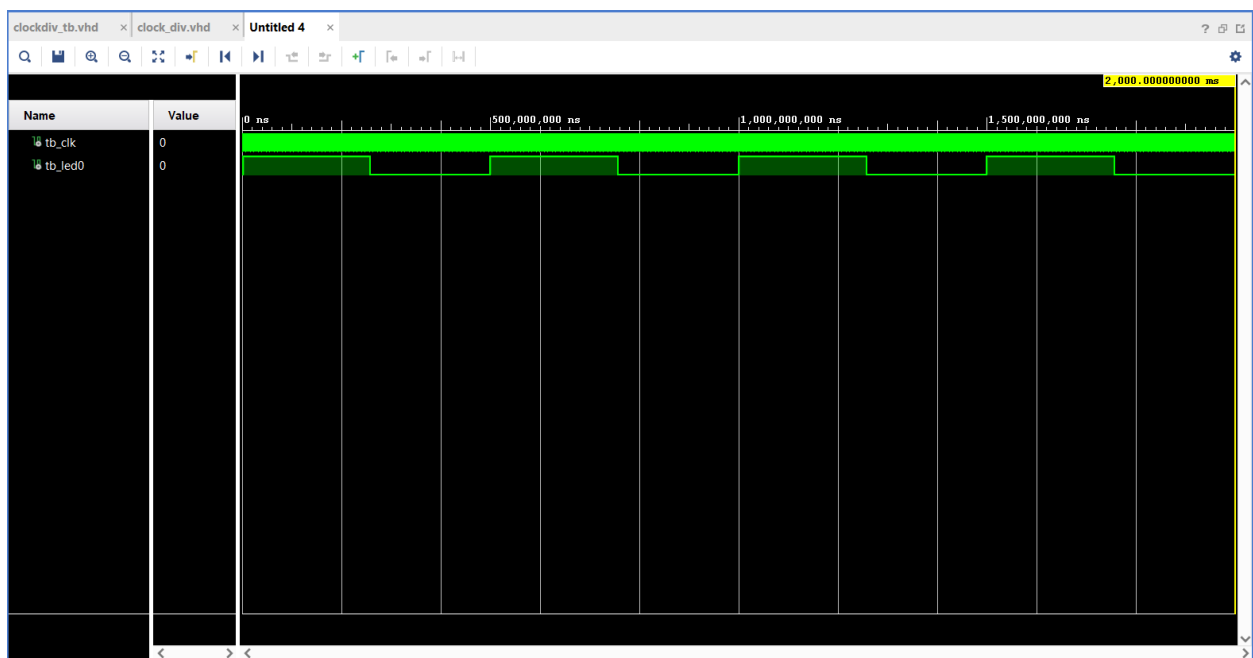Part 1: clock divider

Theory of operation: the clock divider takes a 125MHz input and converts it to a 2Hz clock.

Below are the wave forms for the clock divider. The simulation time was two seconds and the out has a frequency of 2Hz



```
library ieee;
```

```
    use ieee.std_logic_1164.all;
```

```
    use ieee.numeric_std.all;
```

```
entity clock_div is
```

```
    port(
```

```
    clk : in std_logic;  
    div : out std_logic);  
end clock_div;
```

architecture behavior of clock_div is

```
    signal counter : std_logic_vector(26 downto 0) := (others => '0');  
  
begin  
  
    process(clk)  
    begin  
  
        if rising_edge(clk) then  
  
            if (unsigned(counter) < 62499999) then  
                counter <= std_logic_vector(unsigned(counter) + 1);  
  
            else  
                counter <= (others => '0');  
  
            end if;  
  
            if (unsigned(counter) = 31250000) then  
                div <= '1';  
  
            else
```

```
div <= '0';
```


```
end if;
```

```
end if;
```

```
end process;
```

```
end behavior;
```

Divider_top schematic:

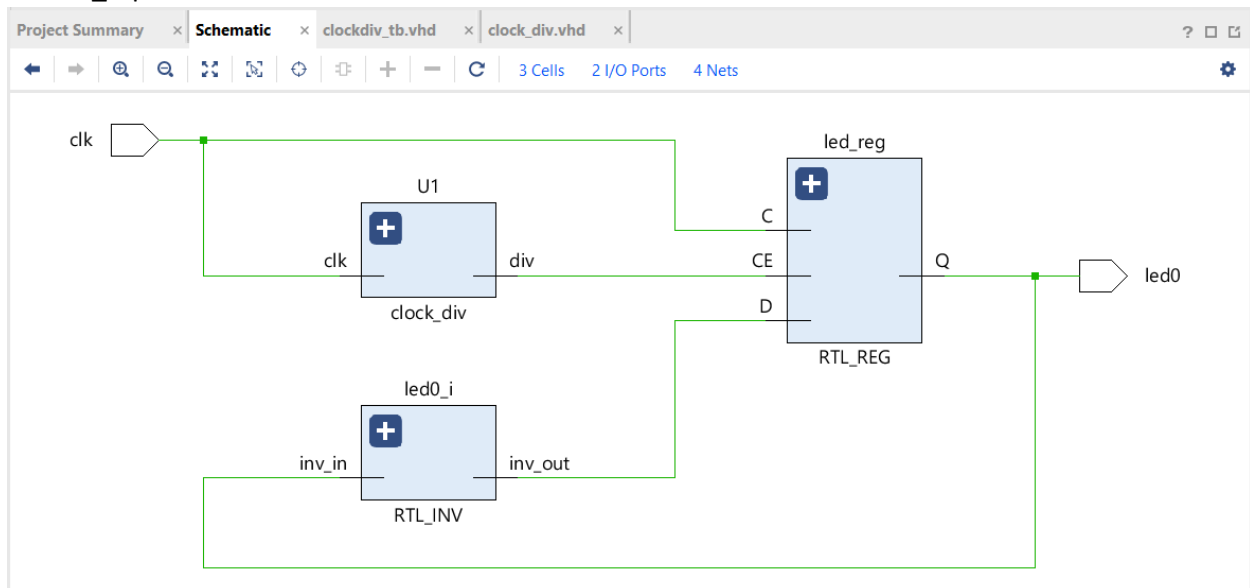

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.numeric_std.all;
```

```
entity RTL_REG is
```

```
port (C, CE, D : in std_logic;
```

```
      Q : out std_logic);
```

```
end RTL_REG;
```

architecture dff of RTL_REG is

begin

process(C)

begin

if C'event and C='1' then

if CE='1' then

Q <= D;

end if;

end if;

end process;

end dff;

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity RTL_INV is

port(inv_in : in std_logic;

inv_out : out std_logic);

end RTL_INV;

architecture inverter of RTL_INV is

begin

inv_out <= not inv_in;

end inverter;

library ieee;

```
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
entity divider_top is  
    port (clk : in std_logic;  
          led0 : out std_logic);  
end divider_top;
```

```
architecture divider_arch of divider_top is
```

```
    component clock_div  
        port(clk : in std_logic;  
              div : out std_logic);  
    end component;
```

```
    component RTL_INV  
        port (inv_in : in std_logic;  
              inv_out : out std_logic);  
    end component;
```

```
    component RTL_REG  
        port (C, CE, D : in std_logic;  
              Q : out std_logic);  
    end component;
```

```
    signal inv_res, led0_out, div_sig : std_logic;
```

```
begin  
    led_reg : RTL_REG  
        port map ( C => clk,
```

```

        CE => div_sig,

        D => inv_res,

        Q => led0_out);

led0_i : RTL_INV

    port map(inv_in => led0_out,

        inv_out => inv_res);


U1 : clock_div

    port map(clk => clk,

        div => div_sig);


led0 <= led0_out;
end divider_arch;

```

TEST BENCH FILE

```

library ieee;

    use ieee.std_logic_1164.all;

    use ieee.numeric_std.all;


entity clkdiv_tb is

end clkdiv_tb;


architecture testbench of clkdiv_tb is


    signal tb_clk : std_logic := '0';


    signal tb_led0 : std_logic;

```

```
component clock_div is
```

```
  port(
```

```
    clk : in std_logic;
```

```
    div : out std_logic
```

```
  );
```

```
end component;
```

```
begin
```

```
  clk_gen_proc: process
```

```
  begin
```

```
    wait for 4 ns;
```

```
    tb_clk <= '1';
```

```
    wait for 4 ns;
```

```
    tb_clk <= '0';
```

```
  end process clk_gen_proc;
```

```
  dut : clock_div
```

```
  port map (
```

```
    clk => tb_clk,
```

```
  ,
```

```
div => tb_led0
```

```
);
```

```
end testbench;
```


Q 1.1) The input needed to be divided by 62500000 (half of 125MHz) in order to get a 2Hz output.

Q 1.2) We would need at least 26 bits for this counter.

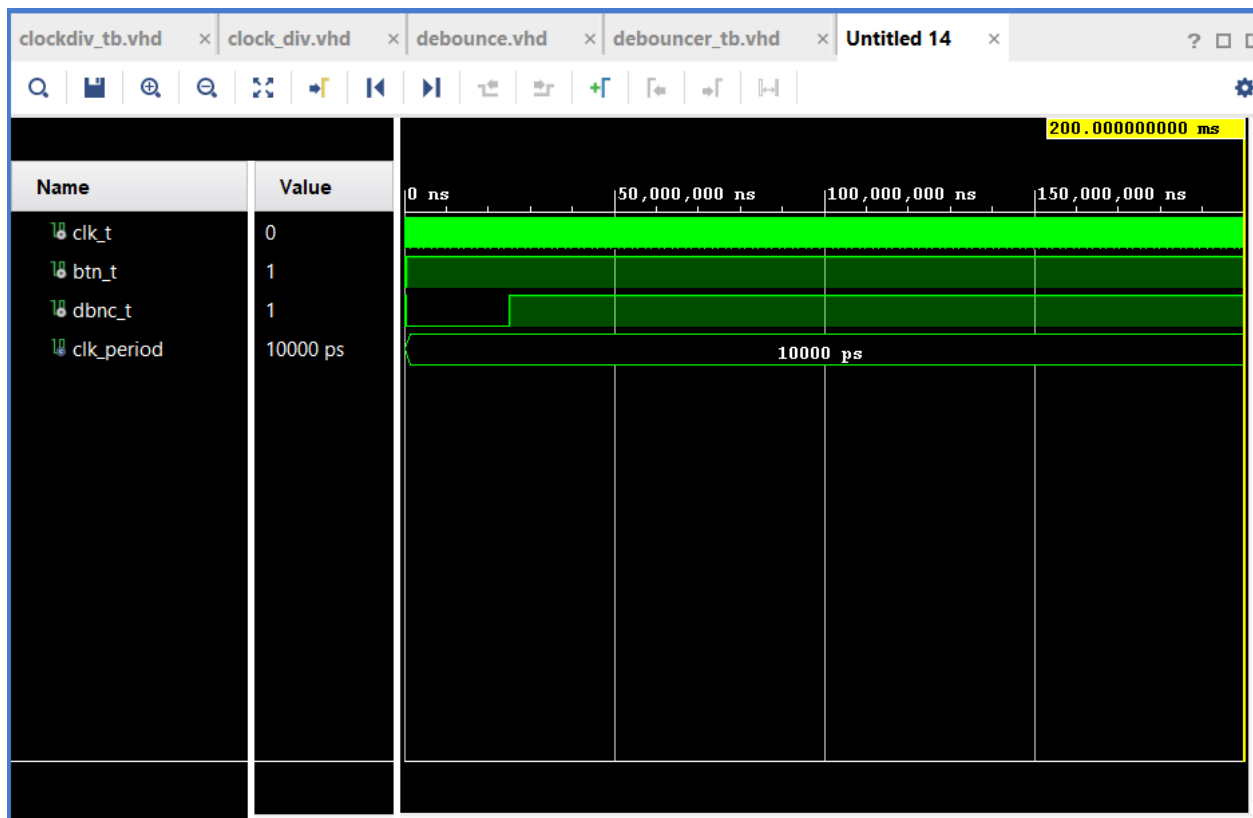Part 2: Debouncer

Theory of Operation: The purpose of the debouncer is to stabilize the signal caused by the press of a button.

Below are the waveforms for the debouncer



Q2.1)The button has an output hi when it is pressed

Q2.3) We need 2.5 million clock ticks for a 20ms debounce time

Q2.4) We need at least 22 bits for this counter

```
library ieee;
    use ieee.std_logic_1164.all;
    use ieee.numeric_std.all;

entity debouncer is
    port ( btn, clk : in std_logic;
          dbnc      : out std_logic);
end debouncer;
architecture debounce of debouncer is
    signal count : std_logic_vector(24 downto 0);
    signal shift_reg : std_logic_vector(1 downto 0);
begin

    process (clk)

    begin
        if clk='1' and clk'event then
            shift_reg(0) <= btn;
            shift_reg(1) <= shift_reg(0);
            if shift_reg(1) = '1' then
                count <= std_logic_vector(unsigned(count) + 1);
                if unsigned(count) < 2500000 then
                    dbnc <= '0';
                else
                    dbnc <= '1';
                end if;
            else
                count <= (others => '0');
                dbnc <= '0';
                -- if btn= not '1' then
                --     count := 0;      --old code
                -- elsif btn='1' then
                --     count := count + 1;
                end if;
            -- end if;

            end if;
        --end if;
    end process;
end debounce;
```

TEST BENCH

```
Library IEEE;
use IEEE.std_logic_1164.all,IEEE.numeric_std.all;
```

```
entity debouncer_tb is
end debouncer_tb;
```

```
architecture tst of debouncer_tb is
Component debouncer
port(clk :in std_logic;
      btn :in std_logic;
      dbnc :out std_logic);
end Component;
```

```
signal clk_t : std_logic := '0';
signal btn_t : std_logic;
signal dbnc_t : std_logic;
```

```
constant clk_period : time := 10 ns;
```

```
begin
uut: debouncer
port map (clk => clk_t,
          btn => btn_t,
          dbnc => dbnc_t);
```

```
clk_p :process
begin
clk_t <= '0';
wait for clk_period/2;
clk_t <= '1';
wait for clk_period/2;
```

```
end process;
```

```
stim_p: process
begin
wait for 100ns;
btn_t<='1';
--wait for 200ns;
--btn_t<='0';
```

```
--wait;  
  
    end process;  
end;
```

Part 3: Fancy Counter

Theory of Operation: For this part we are creating an up/down counter that we can input the maximum value it counts to/resets to when it hits zero.

```
library ieee;  
  
    use ieee.std_logic_1164.all;  
  
    use ieee.numeric_std.all;  
  
entity fancy_counter is  
    port ( clk, clk_en, dir, en, ld, rst, updn : in std_logic;  
          val   : in std_logic_vector(3 downto 0);  
          cnt   : out std_logic_vector(3 downto 0));  
end fancy_counter;
```

architecture fancy_behavior of fancy_counter is

```
    signal direction : std_logic;  
    signal value     : std_logic_vector(3 downto 0);  
    signal count     : std_logic_vector(3 downto 0);  
begin  
    process (clk)
```

```
        begin
```

```
            if clk='1' and clk'event then
```

```
                if en = '1' then
```

```

if rst = '1' then
    cnt <= (others => '0');
    value <= "0000";
    count <= "0000";
elsif clk_en = '1' then
    if updn = '1' then
        direction <= dir;
    end if;
    if ld = '1' then
        value <= val;
    end if;

    if direction = '1' then
        count <= std_logic_vector(unsigned(count) + 1);
        if (count = value) then
            count <= "0000";
        end if;

    elsif direction = '0' then
        count <= std_logic_vector(unsigned(count) - 1);
        if count = "0000" then
            count <= value;
        end if;
    end if;

    cnt <= std_logic_vector(count);
end if;
end if;
end if;
end process;


```

```
end fancy_behavior;
```


Part 4:Bringing it all together

Theory of operation: The counter will have inputs that are operated by buttons whose signals pass through debouncers. The input clock is 2Hz.

Block Diagram

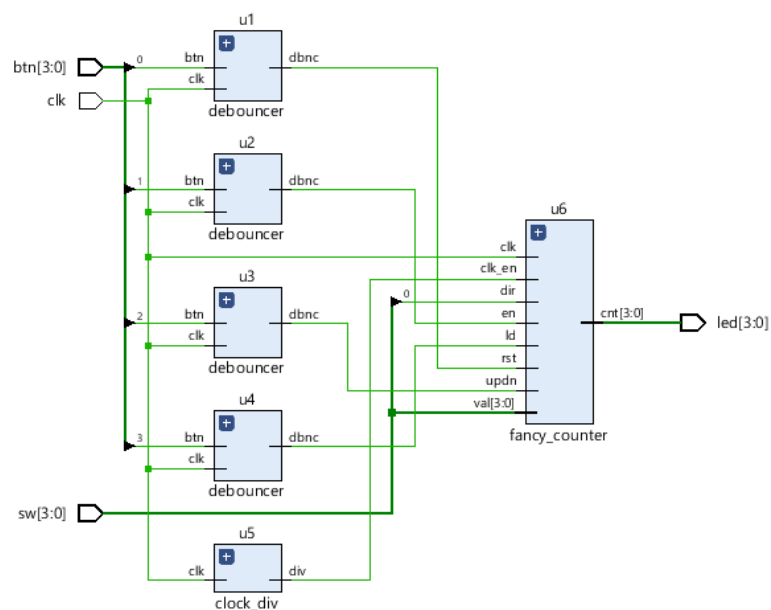

Project summary

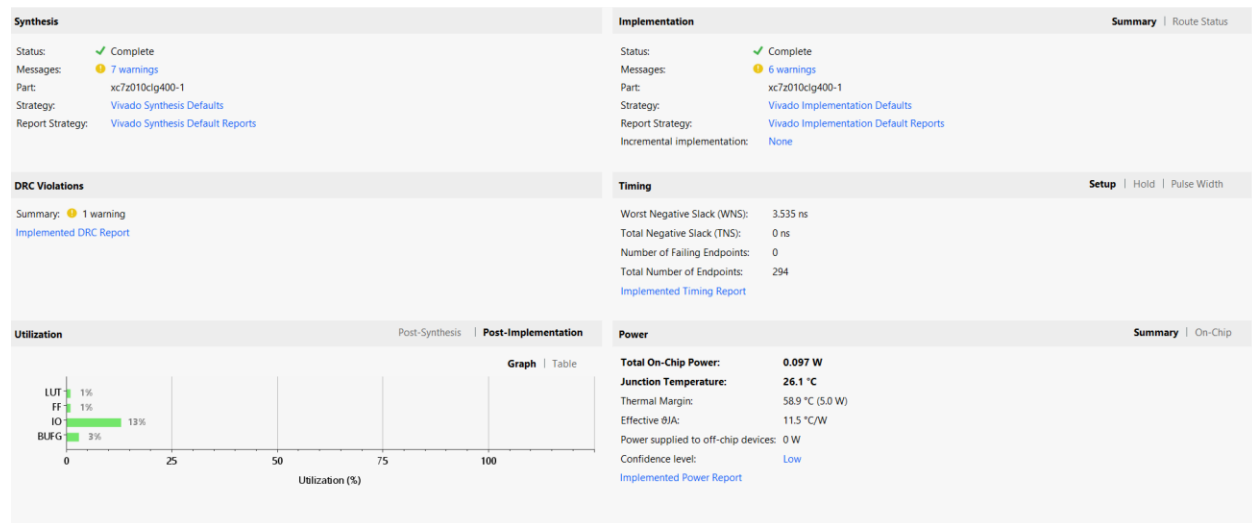

Power analysis

Settings

[Summary \(0.097 W, Margin: N/A\)](#)

Power Supply

Utilization Details

Hierarchical (0.004 W)

Clocks (0.002 W)

Signals (0.001 W)

Data (0.001 W)

Clock Enable (<0.001 W)

Set/Reset (<0.001 W)

Logic (<0.001 W)


I/O (0.002 W)

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.


Total On-Chip Power: **0.097 W**
Design Power Budget: **Not Specified**
Power Budget Margin: **N/A**
Junction Temperature: **26.1 °C**
Thermal Margin: 58.9 °C (5.0 W)
Effective θ JA: 11.5 °C/W
Power supplied to off-chip devices: 0 W
Confidence level: [Low](#)

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Synthesized design

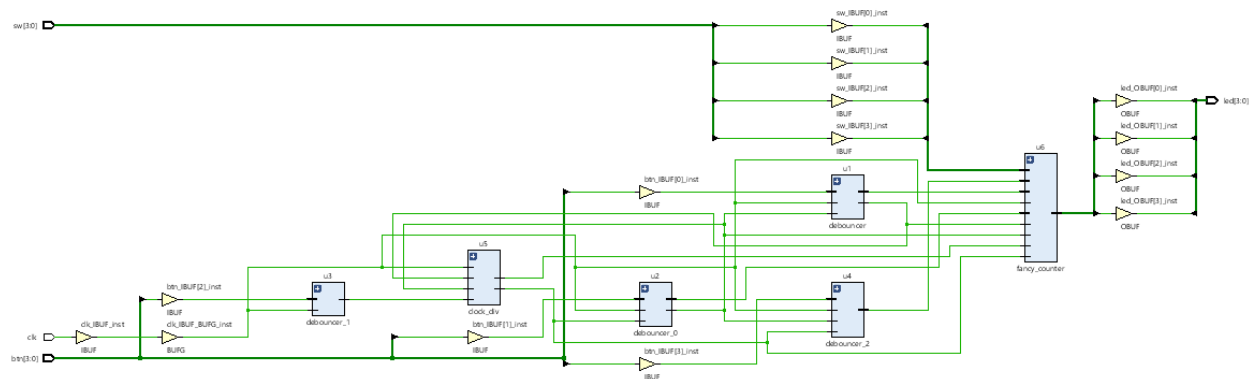

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity counter_top is

port (btn, sw : in std_logic_vector(3 downto 0);

clk : in std_logic;

led : out std_logic_vector(3 downto 0));

end counter_top;

architecture counter_arch of counter_top is

signal dbnc1, dbnc2, dbnc3, dbnc4, div_sig : std_logic;

component debouncer

port (btn, clk : in std_logic;

dbnc : out std_logic);

end component;

component fancy_counter

port (clk, clk_en, dir, en, ld, rst, updn : in std_logic;

```

        val    : in std_logic_vector(3 downto 0);
        cnt    : out std_logic_vector(3 downto 0));
end component;

component clock_div
port(
    clk : in std_logic;
    div : out std_logic);
end component;

begin

u1 : debouncer
    port map (btn => btn(0),
        clk => clk,
        dbnc => dbnc1);

u2 : debouncer
    port map (btn => btn(1),
        clk => clk,
        dbnc => dbnc2);

u3 : debouncer
    port map (btn => btn(2),
        clk => clk,
        dbnc => dbnc3);

u4 : debouncer
    port map (btn => btn(3),
        clk => clk,

```



```
dbnc => dbnc4);
```

```
u5 : clock_div
```

```
port map( clk=> clk,  
          div=>div_sig);
```

```
u6: fancy_counter
```

```
port map (clk  => clk,  
          clk_en => div_sig,  
          dir   => sw(0),  
          en    => dbnc2,  
          ld    => dbnc4,  
          rst   => dbnc1,  
          updn  => dbnc3,  
          val   => sw,  
          cnt   => led);
```

```
end counter_arch;
```

Observations:

In this lab I learned a lot about using the Vivado software and VHDL Logic. In my debouncer, I had to figure out a way to get the counter to stop counting after it reached the desired limit, because the counter would overflow and reset back to zero. This caused a brief flicker in the LEDs which in turn distorted the functionality of my final circuit.